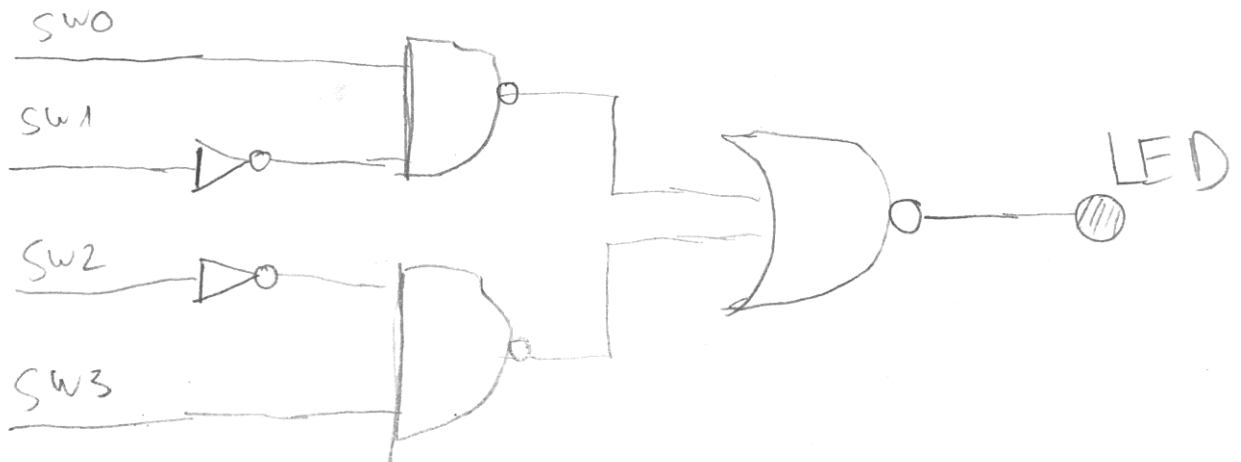


Name: Son Minh Tran

Student ID: 1773429

Lab 2


- 1) Here is the Breadboard Circuit diagram for my last student ID number digit recognizer.



Since I want my circuit to recognize 9 so only need SW0 and SW3 to be on. So the logic will look like this. The whole proof for my design will be like this

$$\begin{aligned} & SW0 \overline{SW1} \overline{SW2} SW3 \\ &= (SW0 \overline{SW1}) (\overline{SW2} SW3) \\ &= \left(((SW0 \overline{SW1}) (\overline{SW2} SW3))' \right)' \\ &= \left(\underbrace{(SW0 \overline{SW1})'}_{\text{NAND}} + \underbrace{(\overline{SW2} SW3)'}_{\text{NAND}} \right)' \\ & \quad \text{NOR} \end{aligned}$$

2)

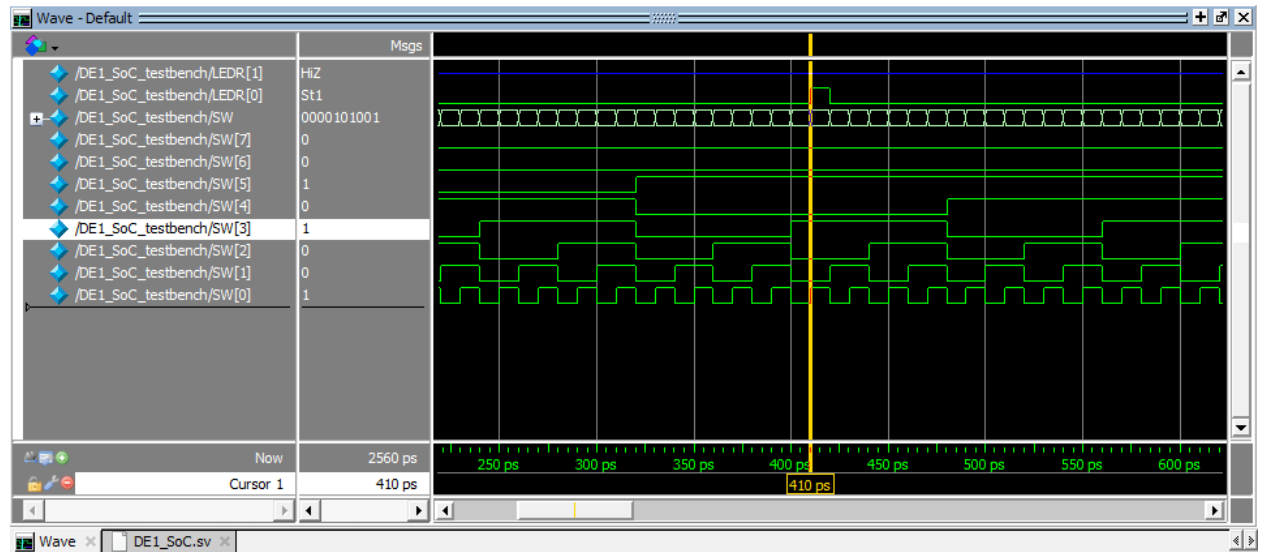

This is the simulation for my last digit circuits recognizer. The test bench will run all the possible case from 0 to 255 in decimal which is from 00000000 to 11111111. The Led output will only be set to 1 if SW[0] SW[3] SW[5] on, all other switch have to be off as the graph shown. This is because my last two digit are 2 and 9 which is encode as 0010 1001 in binary.

3. This lab took me 7 hours in total, including reading, planning, designing, coding, debugging, and testing.